

Notes to class

- Take a look at pset
- More involved derivations, OHI your friend
- Lecture not on test but good for understanding

Lecture Overview

How to use a potentiostat?

How does a potentiostat work?

- Not how a modern one works, but how to visualize it / understand how one could do it. (Mc Guyer)

Background: Intro physics

- IR circuits


$$V = IR$$

$$\sum_{loop} V = 0 \quad \sum_{junction} I = 0$$

Kirchhoff's laws


- Equivalent resistance

- Series

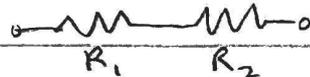


$$R_{eq} = R_1 + R_2$$

- Parallel

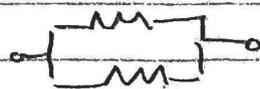

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

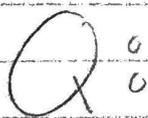

$R_1 \gg R_2$,

Series $R_{eq} = R_1$

Parallel $R_{eq} = R_2$


Definitions

- Galvanometer - measures current (aka ammeter)
- Potentiometer - measures voltage (aka voltmeter)
- Galvanostat - applies a current
- Potentiostat - applies a voltage

How Does Voltmeter work?

- Digital Voltmeters used everywhere (IC)
- Under grad physics!


Draw arrow

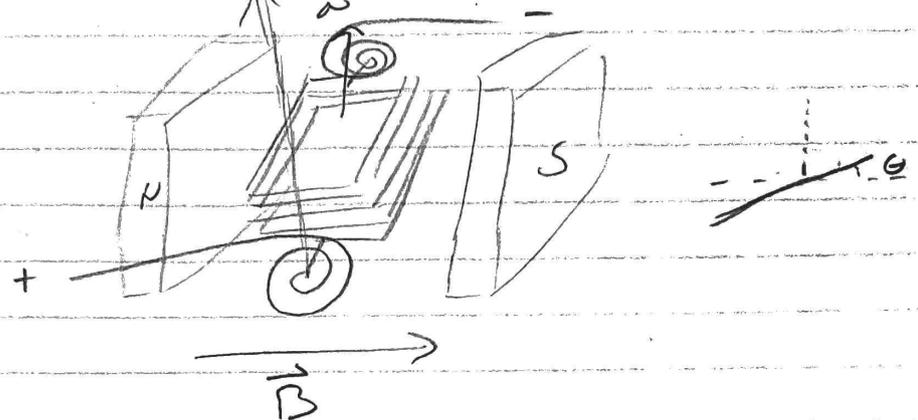

Coil in \vec{B} : $|\vec{\mu}| = nIA$ - (Right hand rule)
 $|\vec{\tau}_{coil}| = |\vec{\mu} \times \vec{B}| = nIA B \sin\theta$
 (actually $\cos\theta$)

Balanced by springs:
 $\tau_{spring} = -\kappa\theta$ (Hooke's law)
 Thin steel wire $\kappa \approx 0.005 \frac{J}{\text{rad}}$

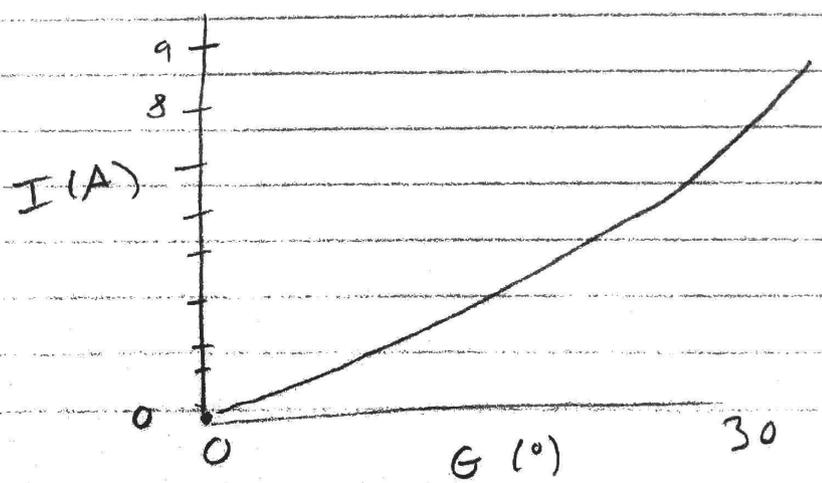Solve: Fridge magnet: $5mT$, use $B = 100mT$
 coil = $10cm \times 10cm = 0.01m^2$
 $\sum \tau = 0 = 20 I (0.01) (0.1) \cos\theta - 0.005 \frac{180}{\pi} \theta$
 $\cos\theta \approx 1$
 $\theta \approx 0.07 I$ (rad)
 $\approx 4 I$ (degrees)



Surprisingly accurate! and linear


d'Arsonval + Repeze 1882

Could detect 0.01 mA

(Wikipedia)


Q: How turn into a volt meter?

- can add large R in series

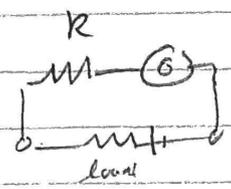

Problem: Draws current unless big, then I too small

Solution:

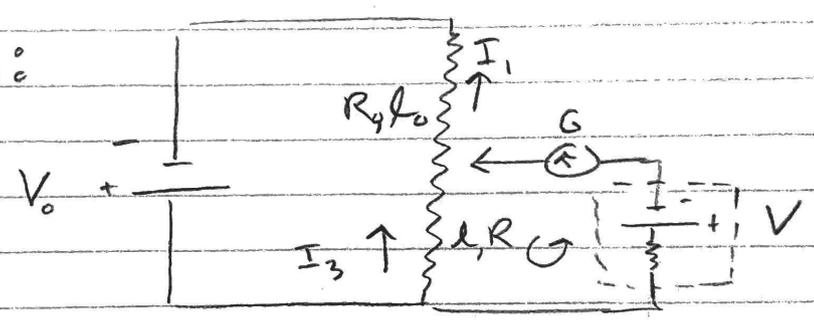


when $I_2 = 0$, $I_1 = I_3 = \frac{V_0}{R_0}$

$$V = I_3 R = \left(\frac{V_0}{R_0}\right) R_0 \left(\frac{l}{l_0}\right) = \left(\frac{V_0}{l_0}\right) l$$

No current through cell and no need to calibrate galvanometer

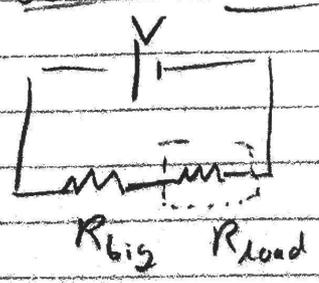Now, assuming we can measure voltage, How to build basic galvanostat



$$I = \frac{V}{R_{big} + R_{load}}$$

IF $R_{big} \gg R_{load}$, $I_{approx} \approx \frac{V}{R_{big}}$

How much bigger does R_{big} need to be for I_{approx} within 1% of I_{real} ?

$$\left| \frac{I_{real} - I_{approx}}{I_{real}} \right| < 0.01$$

$$\left| 1 - \frac{R_{big} + R_{load}}{R_{big}} \right| = \left| \frac{R_{load}}{R_{big}} \right| < 0.01$$

$$R_{big} > 100 R_{load}$$

Voltage applied is fixed, but can change resistance (manually, or through circuit)

Assume $R_{load} < 100 \Omega$

Q. What V needed to apply (within 1%)
 .1 mA, 1 mA, 10 mA? What R_{big} ?

$$R_{big} > 10 \text{ k}\Omega$$


$$R_{big} (10 \text{ mA}) \approx V$$

$$V \approx 100 \text{ V}$$

$$R = 10 \text{ k}\Omega, 100 \text{ k}\Omega, 1 \text{ M}\Omega$$

How to turn into potentiostat?

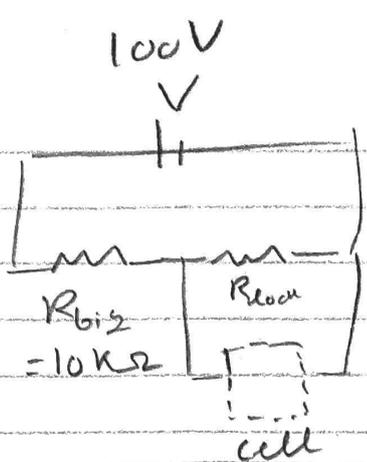- Need known current, but that requires above...
- Not easy, needs high voltage
- IF $R_{load} < 100 \Omega$



$I = 10 \text{ mA}$
 R_{load} can vary to $1 \mu\text{A}$
 $0 - 1 \text{ V}$

But $R_{\text{cell}} < 1 \Omega$


Not EASY

In practice, use op-amps etc.

Potentiostats in real life

- WE, CE, Ref, CA

GAMRY

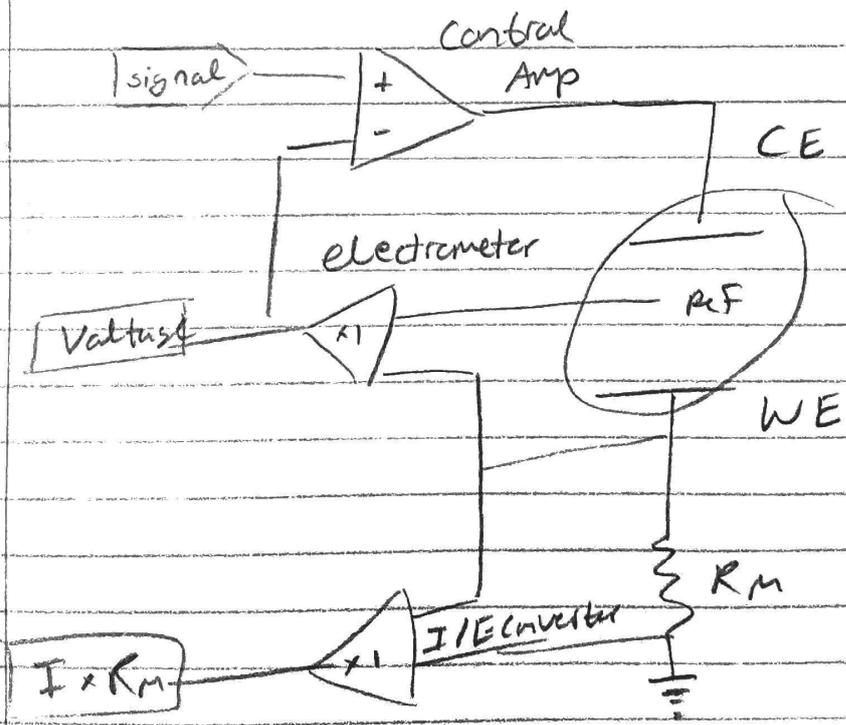


Draw Flow of current

NO I


- Electrometer (high impedance \Rightarrow 0 current)
 - capacitors, etc, to balance w/ circuit to make sure doesn't interfere
 - measures voltage diff
- Current-to-voltage converter
 - measures voltage across known R_m
- Control amplifiers
 - negative feedback loop

APPLY VOLTAGE, MEASURE I
Electrode Setup

CAN USE I as signal too

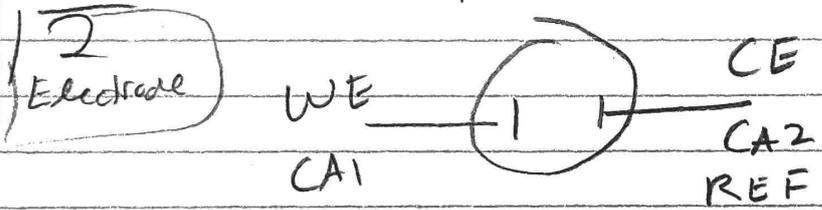

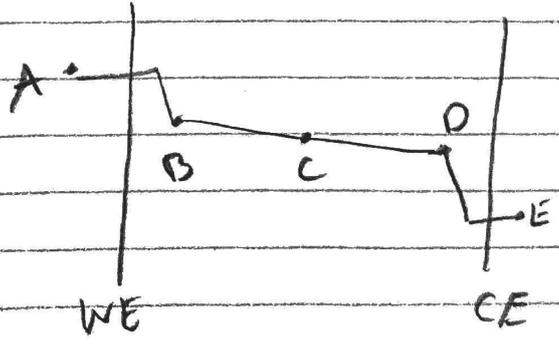
CAN have just 1 CA (Gamm) or both (Biologic)
i.e. Batteries, super capacitors, Fuel cells.



measures $A \leftrightarrow E$


Remember, Voltage at is WE - Ref
But voltage applied is $WE/CA1 - CE/CA2$

3 electrode

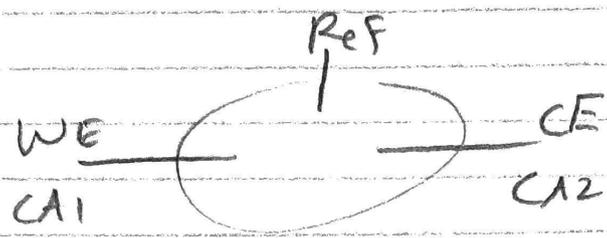

Often what we think of in chem
 COMMON
 Half-cell
 measures $A \leftrightarrow B$

4 electrode

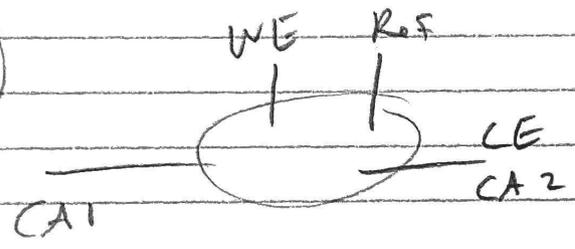

For high solution resistance,
 Want to measure in solution
 (sometimes have CE, sometimes not)

Q: Cell in paper applies 2V
 across whole cell, but I want info on
 just WE, how do I set up if?

CA1, WE, Ref, CE, CA2

or CA1, WE, Ref, CE/CA1

- can only set voltage between WE and Ref
 - can measure between WE + Ref or CE and Ref
 Ref + CE



$$WE - REF = 2V$$

$$WE - CE = WE - REF - (CE - REF)$$

